

Power Plant - Schematics - Templates

Today

- Power Plant?
- Schematics?
- Project Write-up?

Power Supply

- What do we need (voltage and current)? Look at manual for voltage and current for microcontroller and other circuits

Recommended Operating Conditions

Typical values are specified at $V_{CC} = 3.3 \text{ V}$ and $T_A = 25^\circ\text{C}$ (unless otherwise noted)

		MIN	NOM	MAX	UNIT
V_{CC}	Supply voltage during program execution and FRAM programming ($AV_{CC} = DV_{CC}$) ⁽¹⁾	2.0		3.6	V
V_{SS}	Supply voltage ($AV_{SS} = DV_{SS}$)		0		V
T_A	Operating free-air temperature	I version		85	$^\circ\text{C}$
T_J	Operating junction temperature	I version		85	$^\circ\text{C}$
$C_{V_{CORE}}$	Required capacitor at V_{CORE}		470		nF
$C_{V_{CC}}/C_{V_{CORE}}$	Capacitor ratio of V_{CC} to V_{CORE}		10		
f_{SYSTEM}	Processor frequency (maximum MCLK frequency) ⁽²⁾	No FRAM wait states ⁽³⁾ , $2 \text{ V} \leq V_{CC} \leq 3.6 \text{ V}$		8.0	MHz
		With FRAM wait states ⁽³⁾ , $N_{ACCESS} = \{2\}$, $N_{PRECHG} = \{1\}$, $2 \text{ V} \leq V_{CC} \leq 3.6 \text{ V}$		24.0	

- (1) It is recommended to power AV_{CC} and DV_{CC} from the same source. A maximum difference of 0.3 V between AV_{CC} and DV_{CC} can be tolerated during power up and operation.
- (2) Modules may have a different maximum input clock specification. See the specification of the respective module in this data sheet.
- (3) When using manual wait state control, see the *MSP430FR57xx Family User's Guide (SLAU272)* for recommended settings for common system frequencies.

Power Supply

- What do we need (voltage and current)? Look at manual for voltage and current for microcontroller and other circuits

Active Mode Supply Current Into V_{CC} Excluding External Current

over recommended operating free-air temperature (unless otherwise noted) ⁽¹⁾ ⁽²⁾ ⁽³⁾

PARAMETER	EXECUTION MEMORY	V _{CC}	Frequency (f _{MCLK} = f _{SMCLK}) ⁽⁴⁾												UNIT
			1 MHz		4 MHz		8 MHz		16 MHz ⁽⁵⁾		20 MHz ⁽⁵⁾		24 MHz ⁽⁵⁾		
			TYP	MAX	TYP	MAX	TYP	MAX	TYP	MAX	TYP	MAX	TYP	MAX	
I _{AM, FRAM_UNI} ⁽⁶⁾	FRAM	3 V	0.27		0.58		1.0		1.53		1.9		2.2		mA
I _{AM,0%} ⁽⁷⁾	FRAM 0% cache hit ratio	3 V	0.42	0.73	1.2	1.6	2.2	2.8	2.3	2.9	2.8	3.6	3.45	4.3	mA
I _{AM,50%} ^{(7) (8)}	FRAM 50% cache hit ratio	3 V	0.31		0.73		1.3		1.75		2.1		2.5		
I _{AM,66%} ^{(7) (8)}	FRAM 66% cache hit ratio	3 V	0.27		0.58		1.0		1.55		1.9		2.2		
I _{AM,75%} ^{(7) (8)}	FRAM 75% cache hit ratio	3 V	0.25		0.5		0.82		1.3		1.6		1.8		
I _{AM,100%} ^{(7) (8)}	FRAM 100% cache hit ratio	3 V	0.2	0.43	0.3	0.55	0.42	0.8	0.73	1.15	0.88	1.3	1.0	1.5	
I _{AM, RAM} ^{(8) (9)}	RAM	3 V	0.2	0.4	0.35	0.55	0.55	0.75	1.0	1.25	1.20	1.45	1.45	1.75	mA

Power Supply

- What do we need (voltage and current)? Look at manual for voltage and current for microcontroller and other circuits

- All inputs are tied to 0 V or to V_{CC} . Outputs do not source or sink any current.
- The currents are characterized with a Micro Crystal CC4V-T1A SMD crystal with a load capacitance of 9 pF. The internal and external load capacitance are chosen to closely match the required 9 pF.
- Characterized with program executing typical data processing.
- At MCLK frequencies above 8 MHz, the FRAM requires wait states. When wait states are required, the effective MCLK frequency, $f_{MCLK,eff}$, decreases. The effective MCLK frequency is also dependent on the cache hit ratio. SMCLK is not affected by the number of wait states or the cache hit ratio. The following equation can be used to compute $f_{MCLK,eff}$:

$$f_{MCLK,eff,MHZ} = f_{MCLK,MHZ} \times 1 / [\# \text{ of wait states} \times ((1 - \text{cache hit ratio percent}/100)) + 1]$$
- MSP430FR573x series only
- Program and data reside entirely in FRAM. No wait states enabled. DCORSEL = 0, DCOFSELx = 3 ($f_{DCO} = 8 \text{ MHz}$). MCLK = SMCLK.
- Program resides in FRAM. Data resides in SRAM. Average current dissipation varies with cache hit-to-miss ratio as specified. Cache hit ratio represents number cache accesses divided by the total number of FRAM accesses. For example, a 25% ratio implies one of every four accesses is from cache, the remaining are FRAM accesses.
 For 1, 4, and 8 MHz, DCORSEL = 0, DCOFSELx = 3 ($f_{DCO} = 8 \text{ MHz}$). MCLK = SMCLK. No wait states enabled.
 For 16 MHz, DCORSEL = 1, DCOFSELx = 0 ($f_{DCO} = 16 \text{ MHz}$). MCLK = SMCLK. One wait state enabled.
 For 20 MHz, DCORSEL = 1, DCOFSELx = 2 ($f_{DCO} = 20 \text{ MHz}$). MCLK = SMCLK. Three wait states enabled.
 For 24 MHz, DCORSEL = 1, DCOFSELx = 3 ($f_{DCO} = 24 \text{ MHz}$). MCLK = SMCLK. Three wait states enabled.
- See [Figure 1](#) for typical curves. Each characteristic equation shown in the graph is computed using the least squares method for best linear fit using the typical data shown in [Active Mode Supply Current Into \$V_{CC}\$ Excluding External Current](#).
 $f_{ACLK} = 32786 \text{ Hz}$, $f_{MCLK} = f_{SMCLK}$ at specified frequency. No peripherals active.
 $XTS = CPUOFF = SCG0 = SCG1 = OSCOFF = SMCLKOFF = 0$.
- All execution is from RAM.
 For 1, 4, and 8 MHz, DCORSEL = 0, DCOFSELx = 3 ($f_{DCO} = 8 \text{ MHz}$). MCLK = SMCLK.
 For 16 MHz, DCORSEL = 1, DCOFSELx = 0 ($f_{DCO} = 16 \text{ MHz}$). MCLK = SMCLK.
 For 20 MHz, DCORSEL = 1, DCOFSELx = 2 ($f_{DCO} = 20 \text{ MHz}$). MCLK = SMCLK.
 For 24 MHz, DCORSEL = 1, DCOFSELx = 3 ($f_{DCO} = 24 \text{ MHz}$). MCLK = SMCLK.

Power Supply

- Where do we get the power?
- Plug into wall
 - Wall - Need to drop 120 VAC to Low Voltage VDC
 - Transformer-based
 - Switching
- Use batteries
 - Battery Voltage changes with discharge
 - Conversion from variable voltage to constant voltage
 - Regulator
 - Switcher


Batteries

- Battery $\equiv >1$ cell
- Cell can be modeled as ideal voltage source with a series resistance
 - Series resistance induces a voltage drop as current rises
- How long will it last?
 - Cells can be modeled as having a constant capacity (1 amp-hour = 3600 coulombs = 3600 amp-seconds) (*less accurate*)
 - Battery life (hours) = capacity (amp-hours)/current (amps)
 - Can also predict life based on discharge plot (*more accurate*)
- What if voltage or current isn't right?
 - Can put cells in series (add voltages) or parallel (add currents)
 - Can use a voltage regulator (linear or switch-mode)

Battery Power


- A 800 mAhr battery will power a device that draws 200mA for how long?
 $800 \text{ mAhr} / 200\text{mA} = 4 \text{ hr}$
- What is the voltage of a “AA” battery?
- What is the current capabilities?

Battery Power

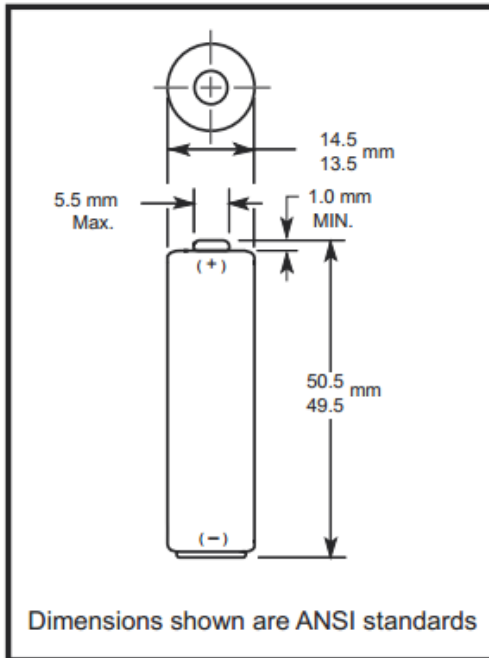


Nominal Voltage:	1.5 V
Operating Voltage	1.6 - 0.75V
Impedance:	81 m-ohm @ 1kHz
Typical Weight:	24 gm (0.8 oz.)
Typical Volume:	8.4 cm ³ (0.5 in. ³)
Terminals:	Flat
Storage Temperature Range:	-20 ^o C to 35 ^o C
Operating Temperature Range:	-20 ^o C to 54 ^o C (-4 ^o F to 130 ^o F)
ANSI:	15A
IEC:	LR6

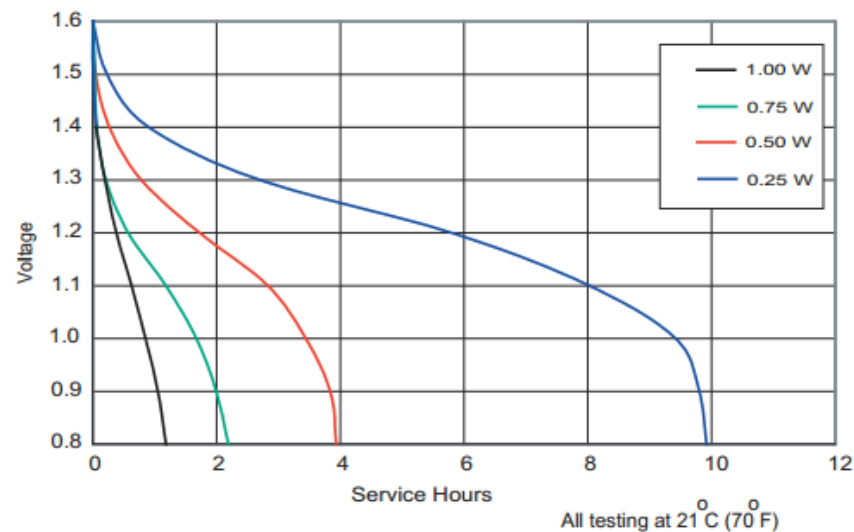
TYPICAL DISCHARGE CHARACTERISTICS AT VARIOUS POWER DRAINS



Battery Power

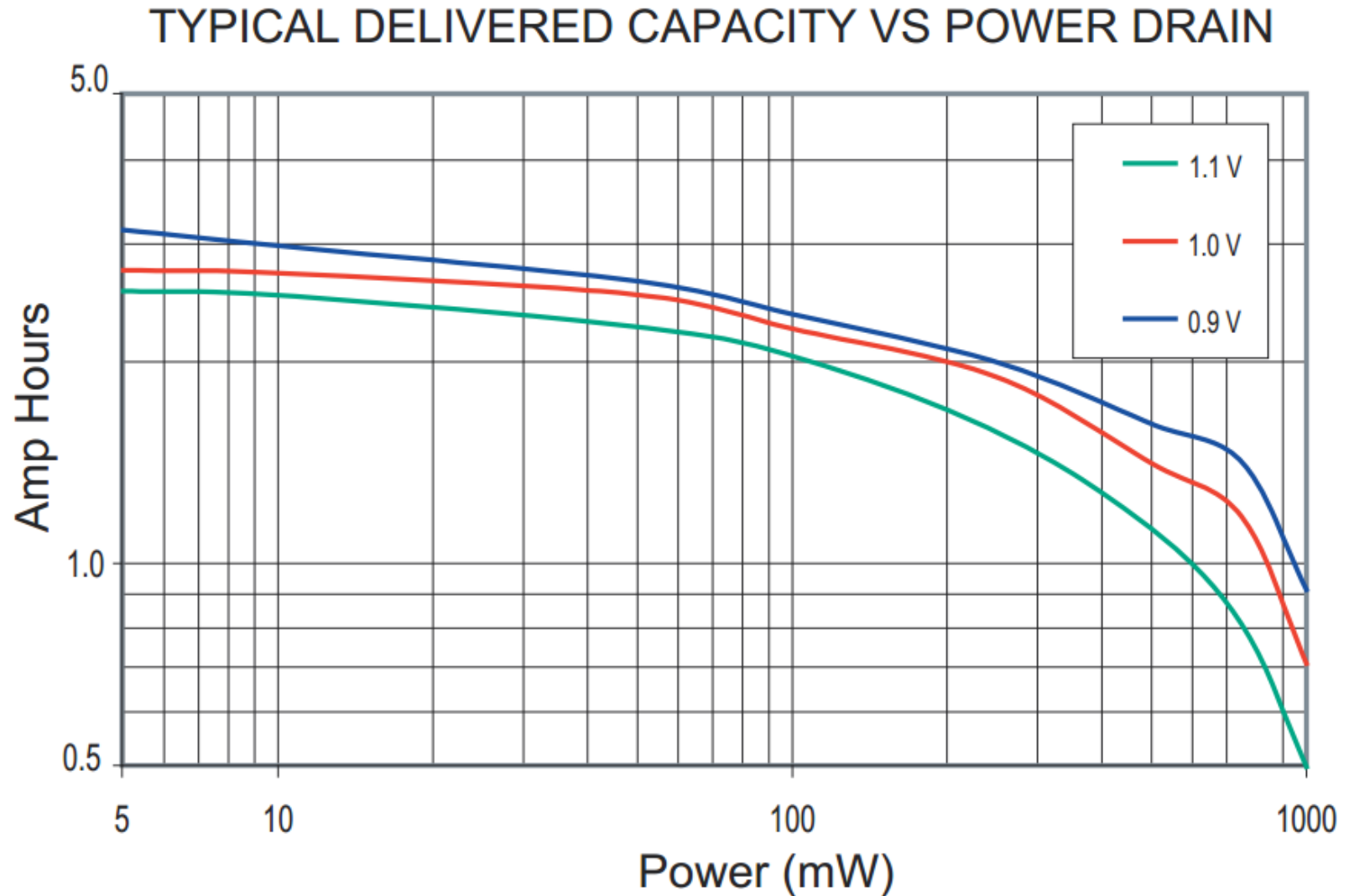

Battery Power

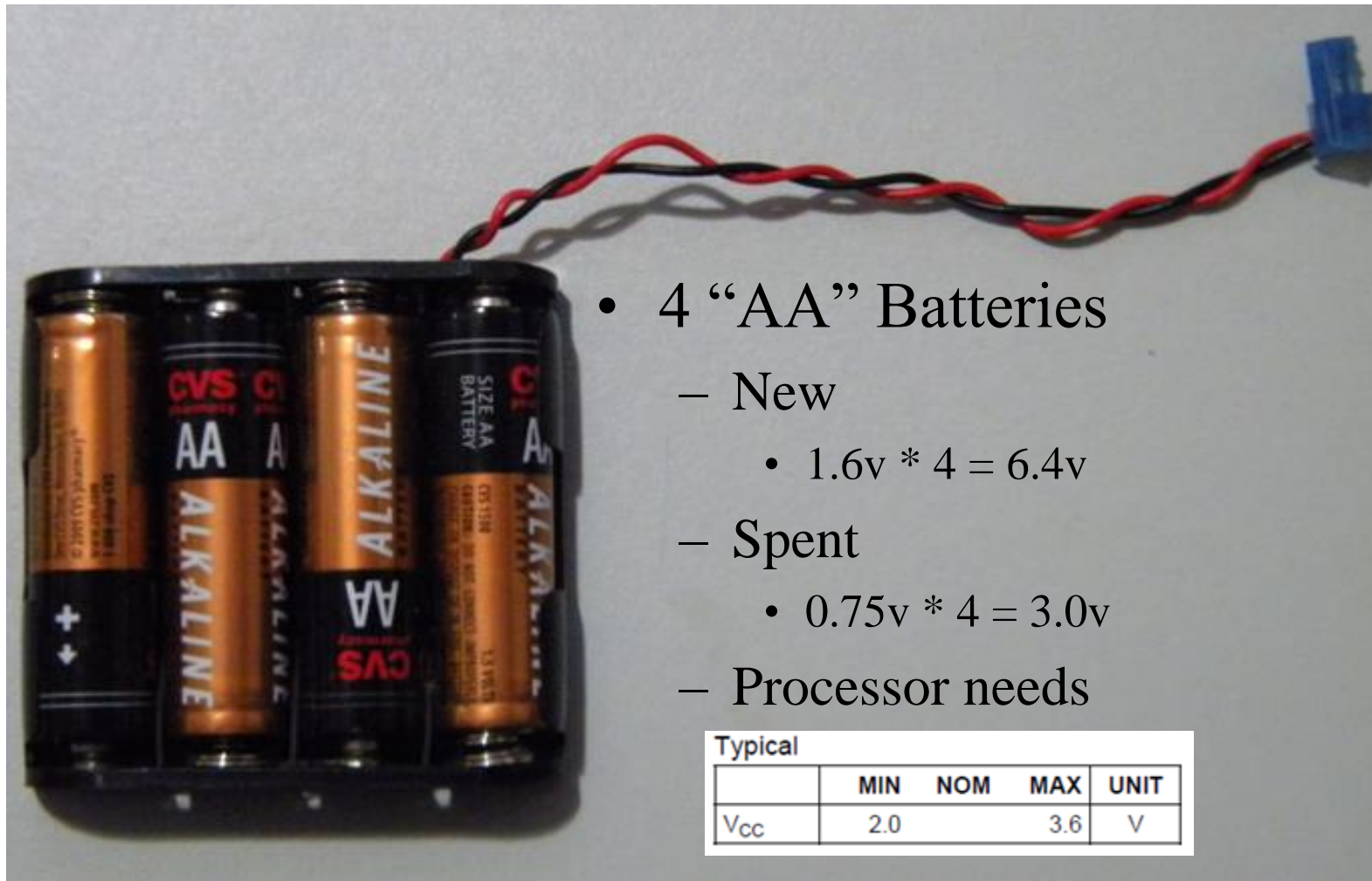


- 4 “AA” Batteries
 - New
 - $1.6\text{v} * 4 = 6.4\text{v}$
 - Spent
 - $0.75\text{v} * 4 = 3.0\text{v}$
 - Processor needs

Typical

	MIN	NOM	MAX	UNIT
V _{cc}	2.0		3.6	V

Battery Power

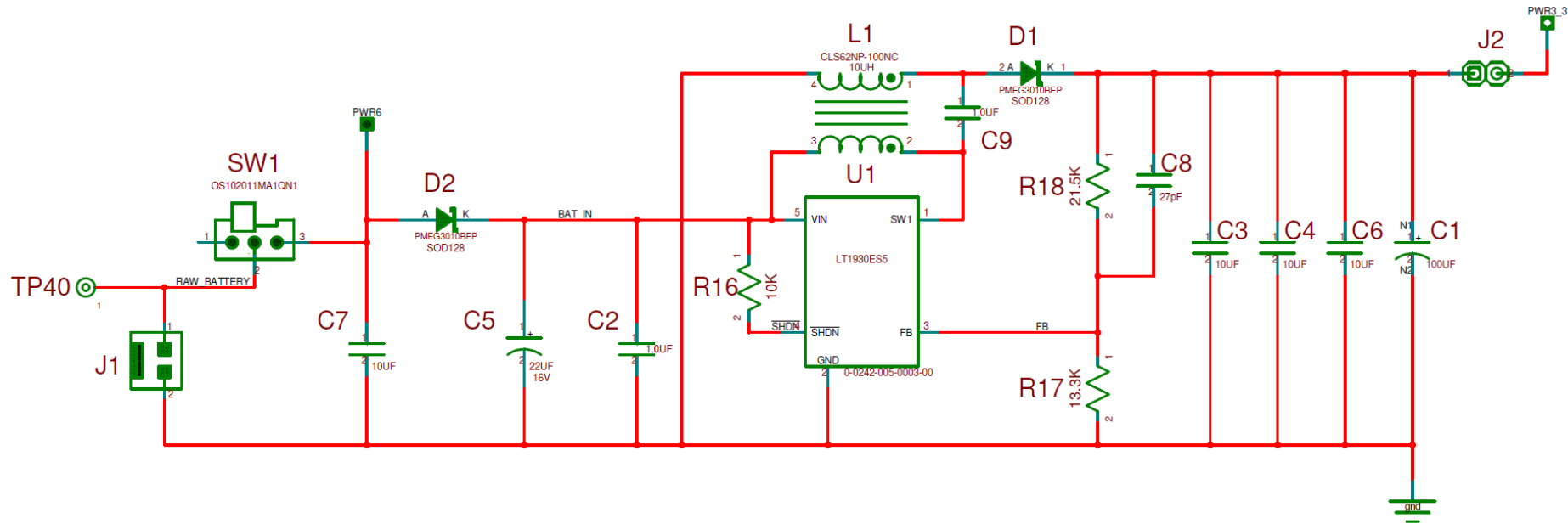

Boost Converter as Sepic Converter

Battery Power

Single Inductor

Regulated Output with Input Voltages

Above, Below or Equal to the Output

Wide VIN Range: 2.6V to 16V


VOUT Range: 2.4V to 5.25V

Low Shutdown Current: <1uA

Low Profile (1mm) ThinSOT Package

Battery Power


■ Wide VIN Range: 2.6V to 16V

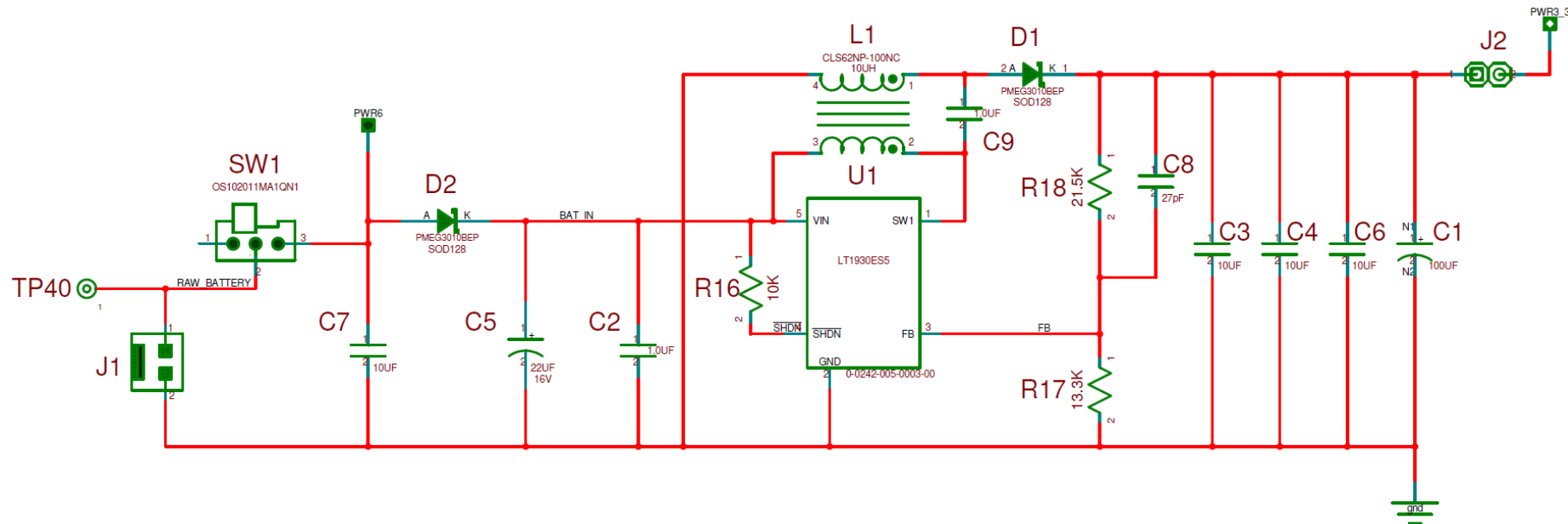

Battery Power

■ Wide VIN Range: 2.6V to 16V


4 “AA” Batteries ~ 6v

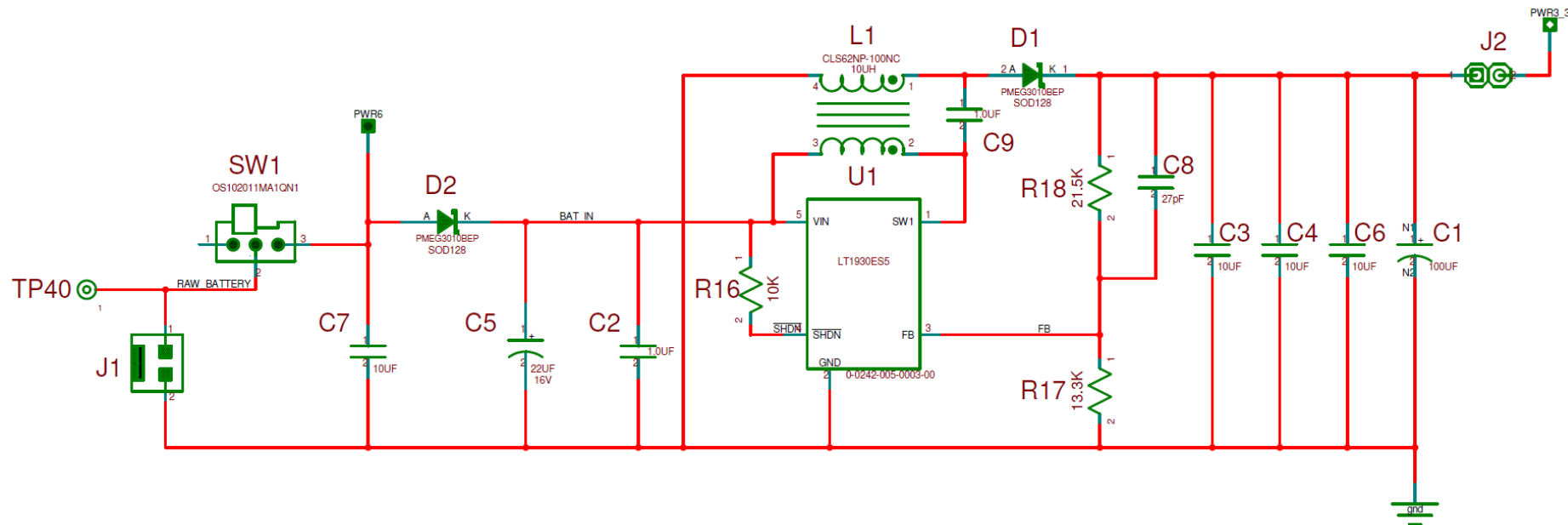

Battery Power

■ Wide VIN Range: 2.6V to 16V

4 “AA” Batteries ~ 6v

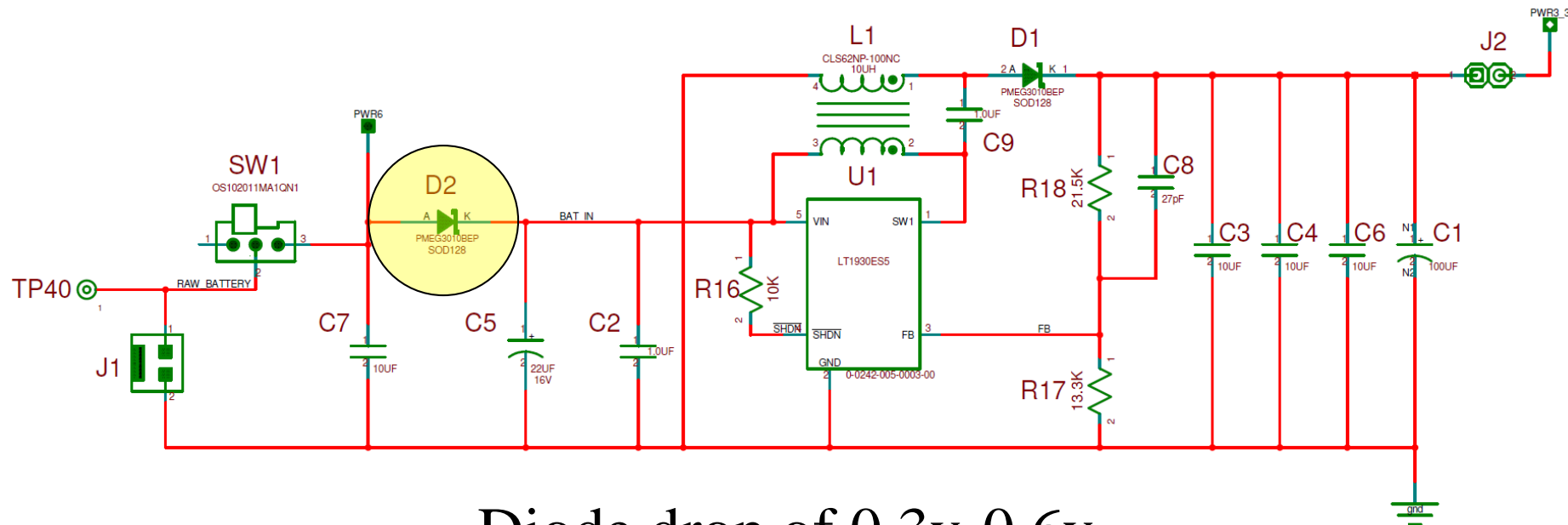


Diode drop of 0.3v-0.6v

P-FET drop 0.1-0.3v


Protection against Batteries installed backward

Battery Power

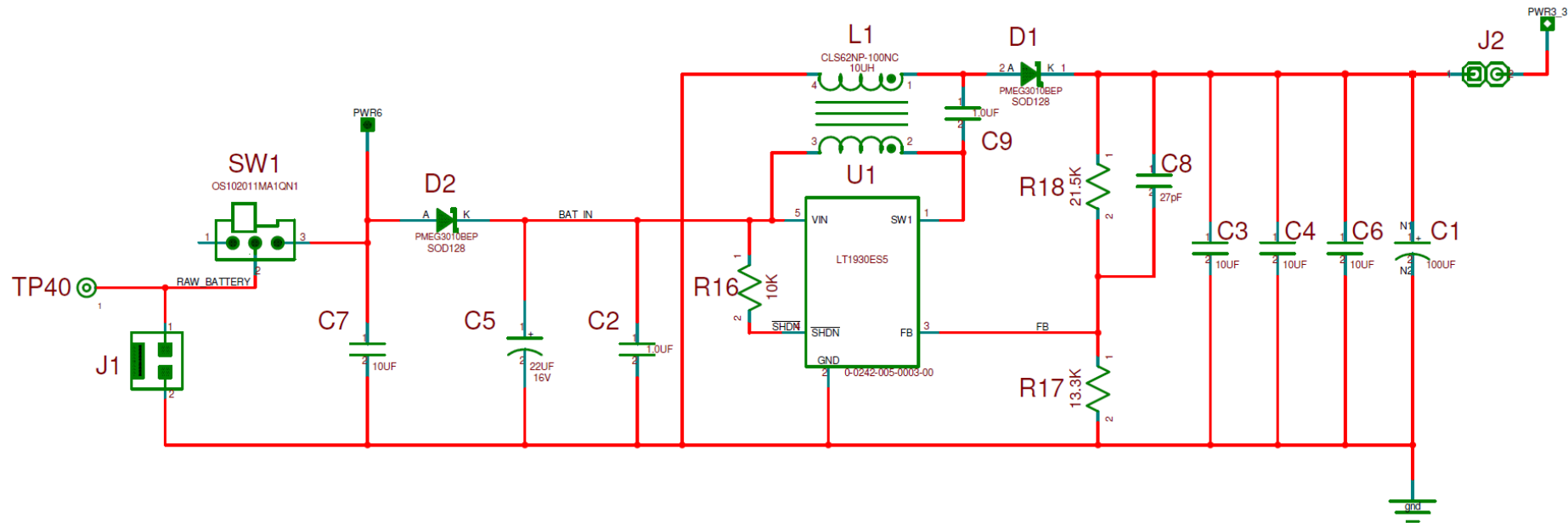■ Synchronous Rectification: Up to 87% Efficiency




Battery Power

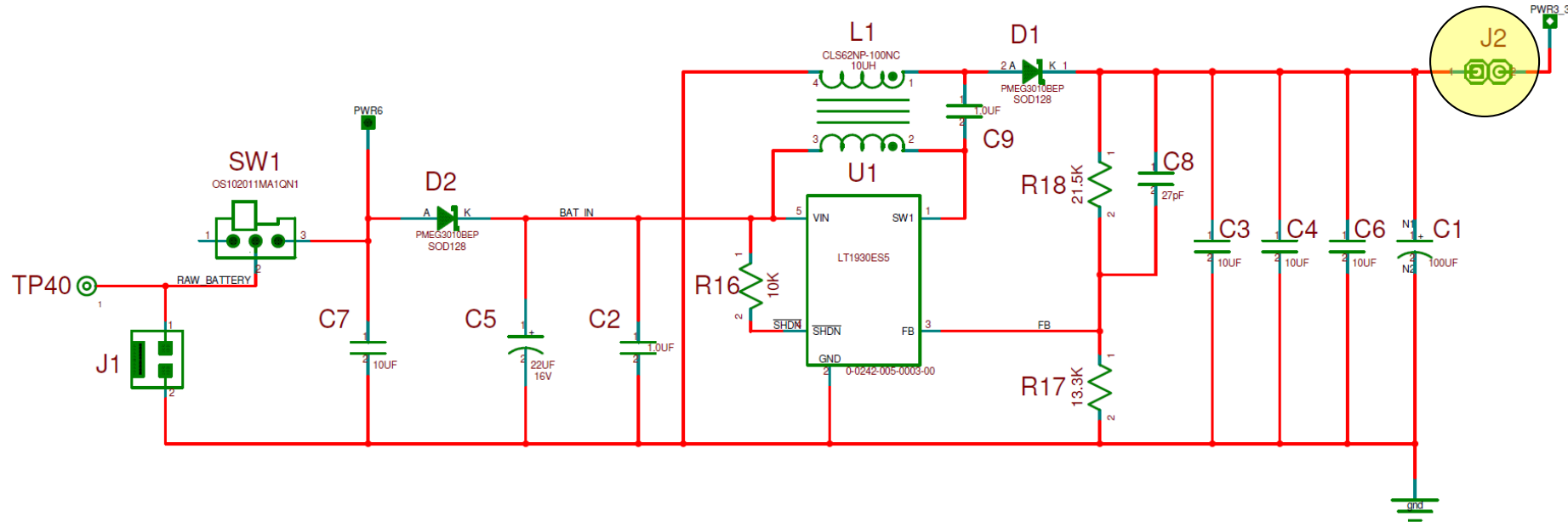


If you measure the current into the load
as 31ma, measured at J2.
How long will the batteries last with
continuous use?

Battery Power

Efficiency

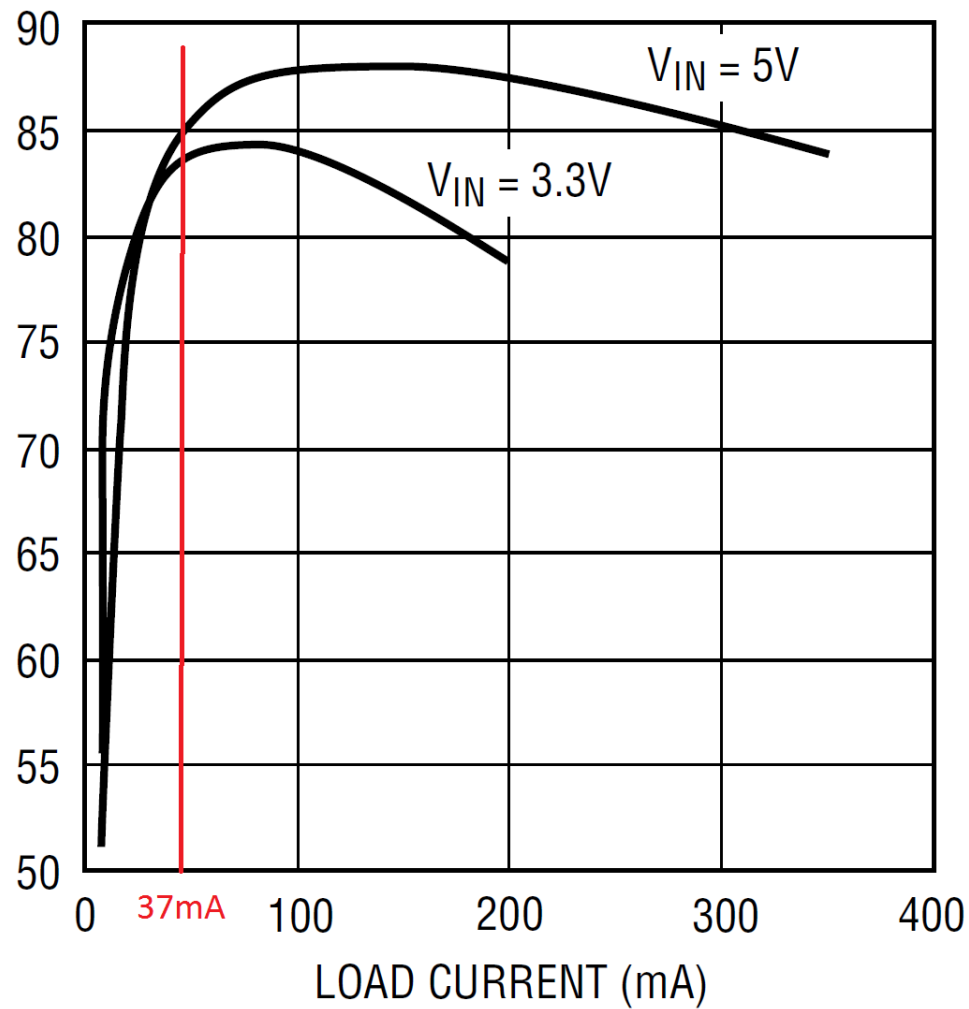

Battery Power

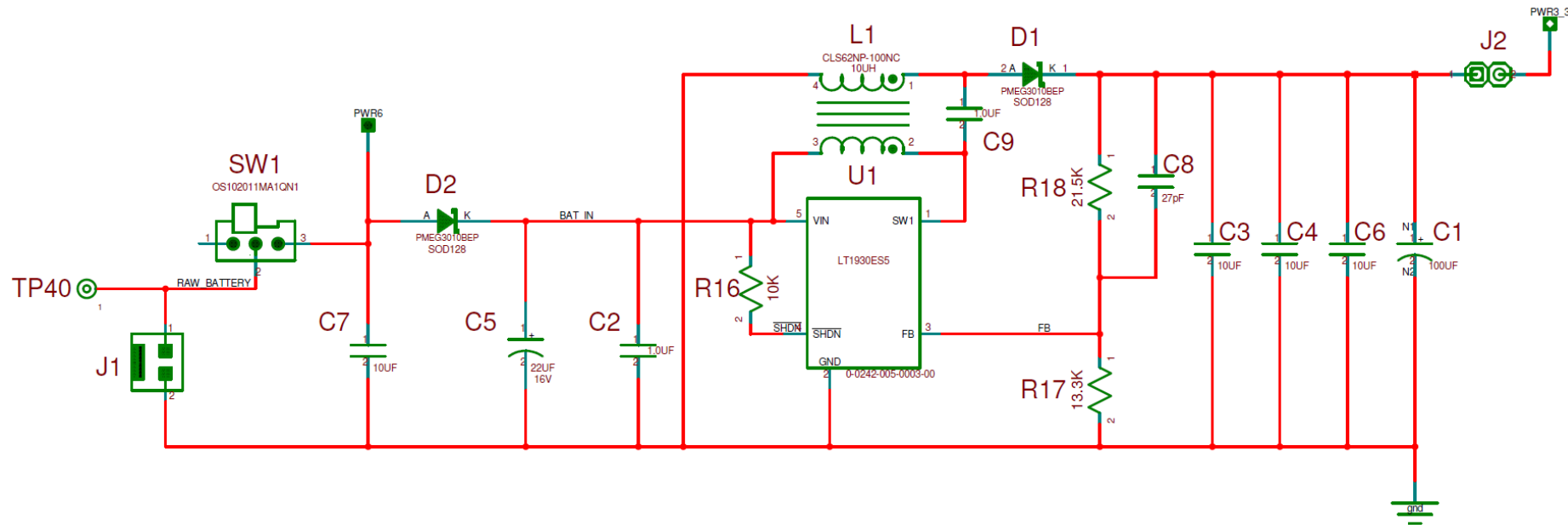


Voltage = Current * Resistance

Power = Voltage * Current

Battery Voltage changes – What about current?

How can you solve this problem?

Battery Power

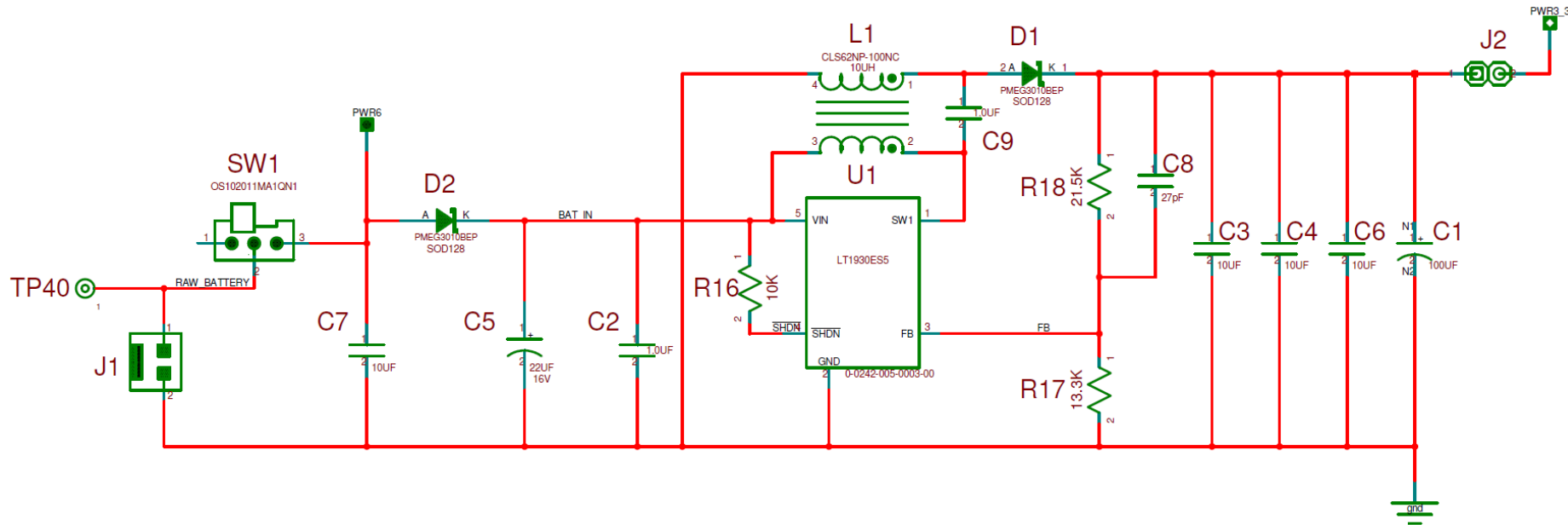


Voltage = 3.3v Current = 31mA

Power = 3.3v * 31mA ➔ 102.3mW

Battery Power

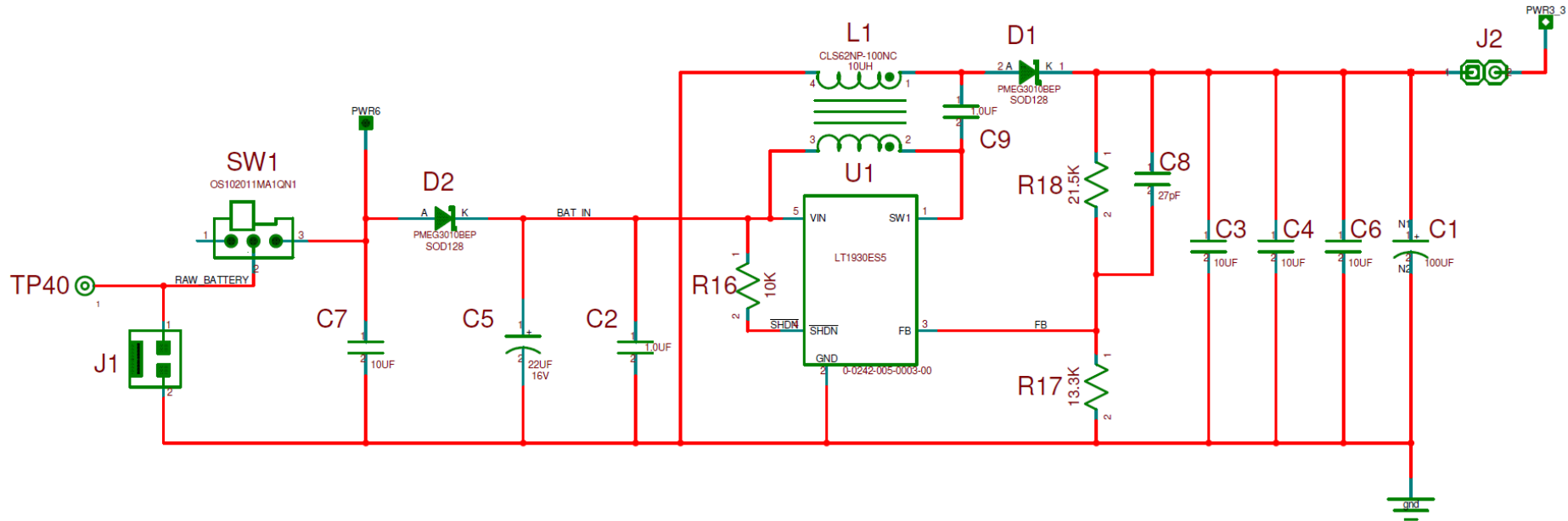■ Synchronous Rectification: From Graph ~85% Efficient



Voltage = 3.3v Current = 31mA


Power = 3.3v * 31mA ➔ 102.3mW

102.3 mW / 85% efficiency = 120.35mW from Batteries


With 4 Batteries –

120.35mW / 4 batteries = 30.09mW per battery

Battery Power

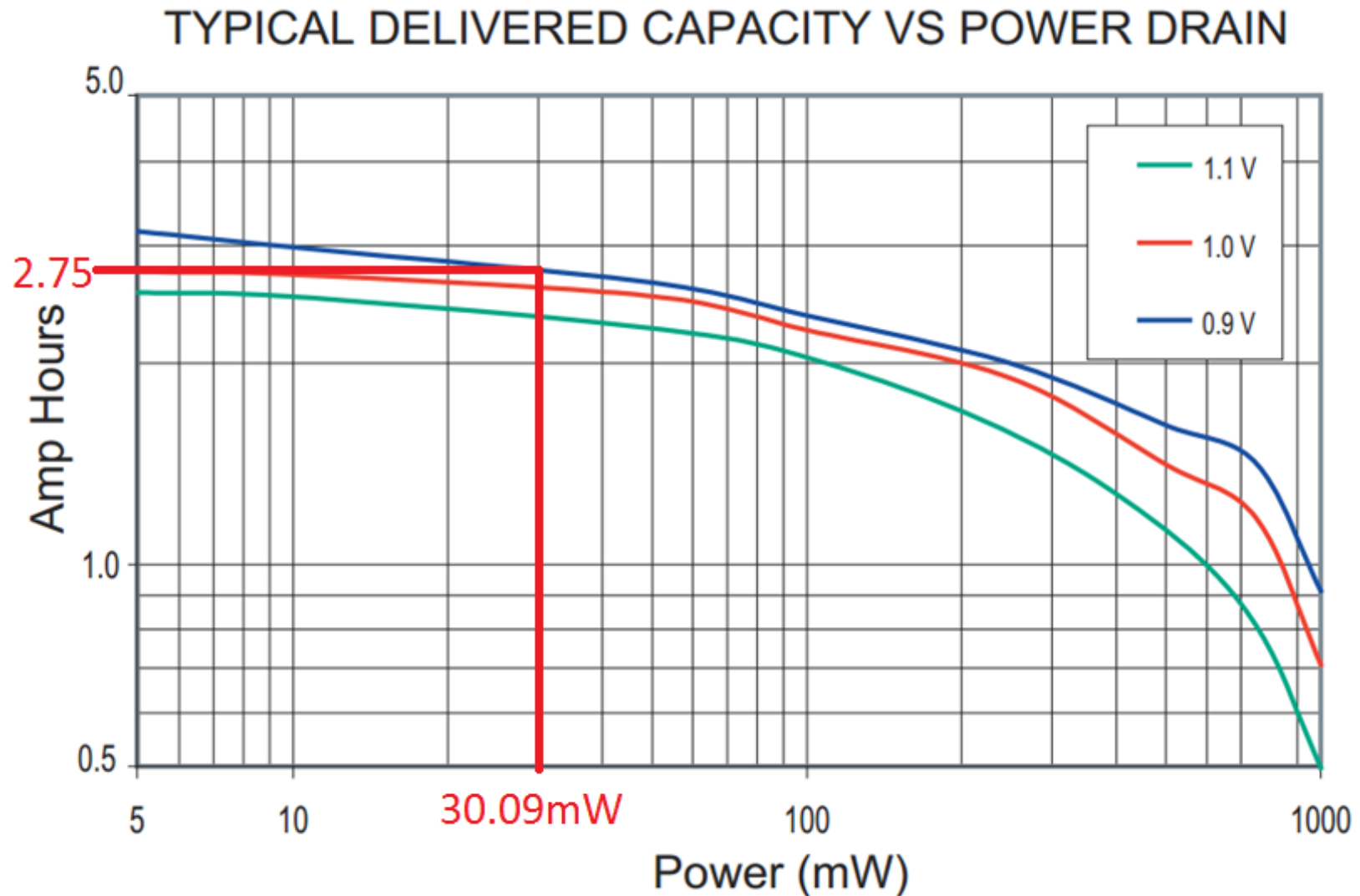


Battery Power

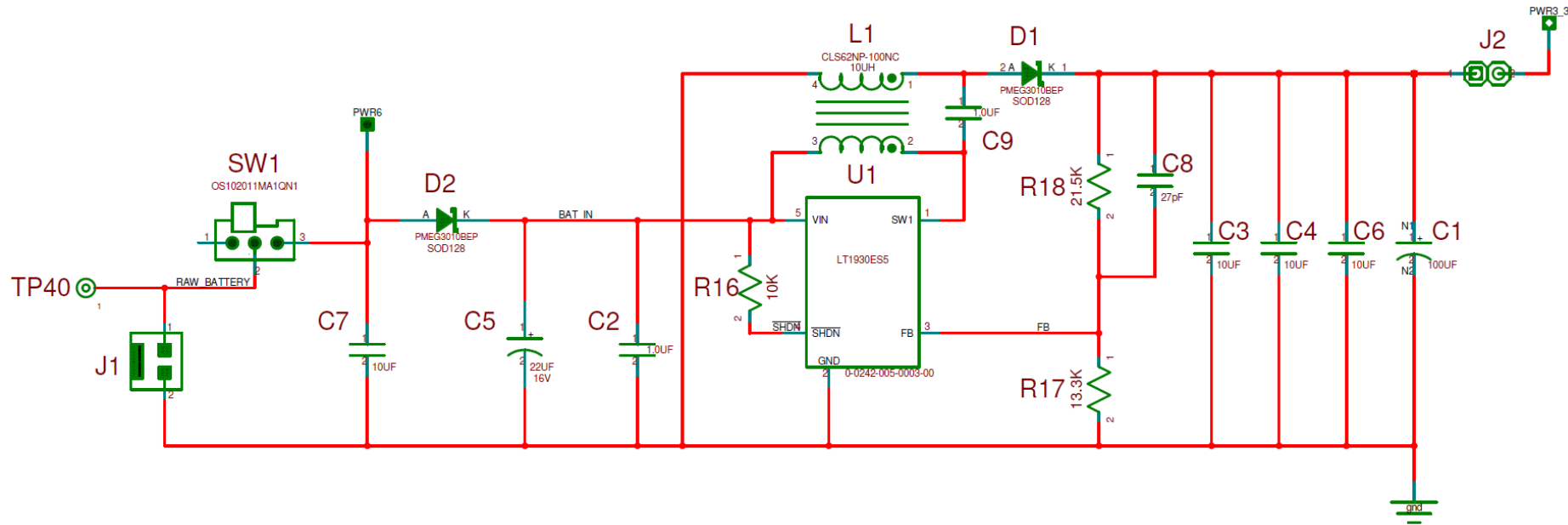


$$\text{Time} = 2.75 \text{ Amp-Hour} / 0.031 \text{ Amp} = \mathbf{88.7 \text{ Hours}}$$

Schematics

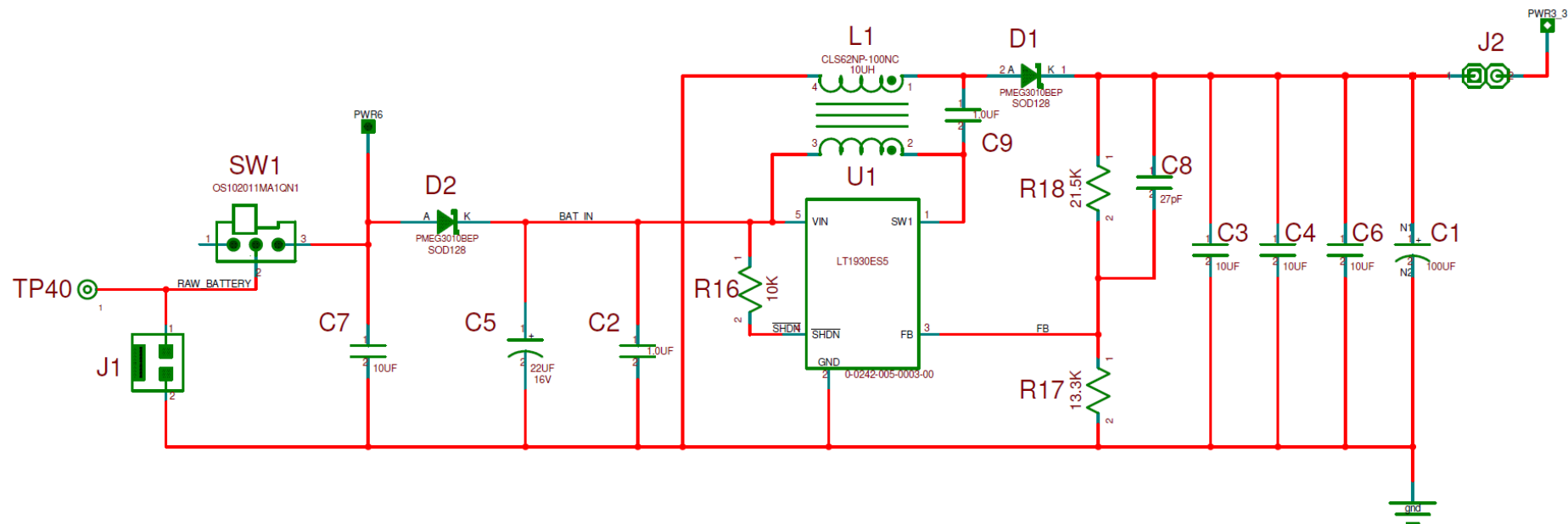


Schematics

Right Motor H-Bridge

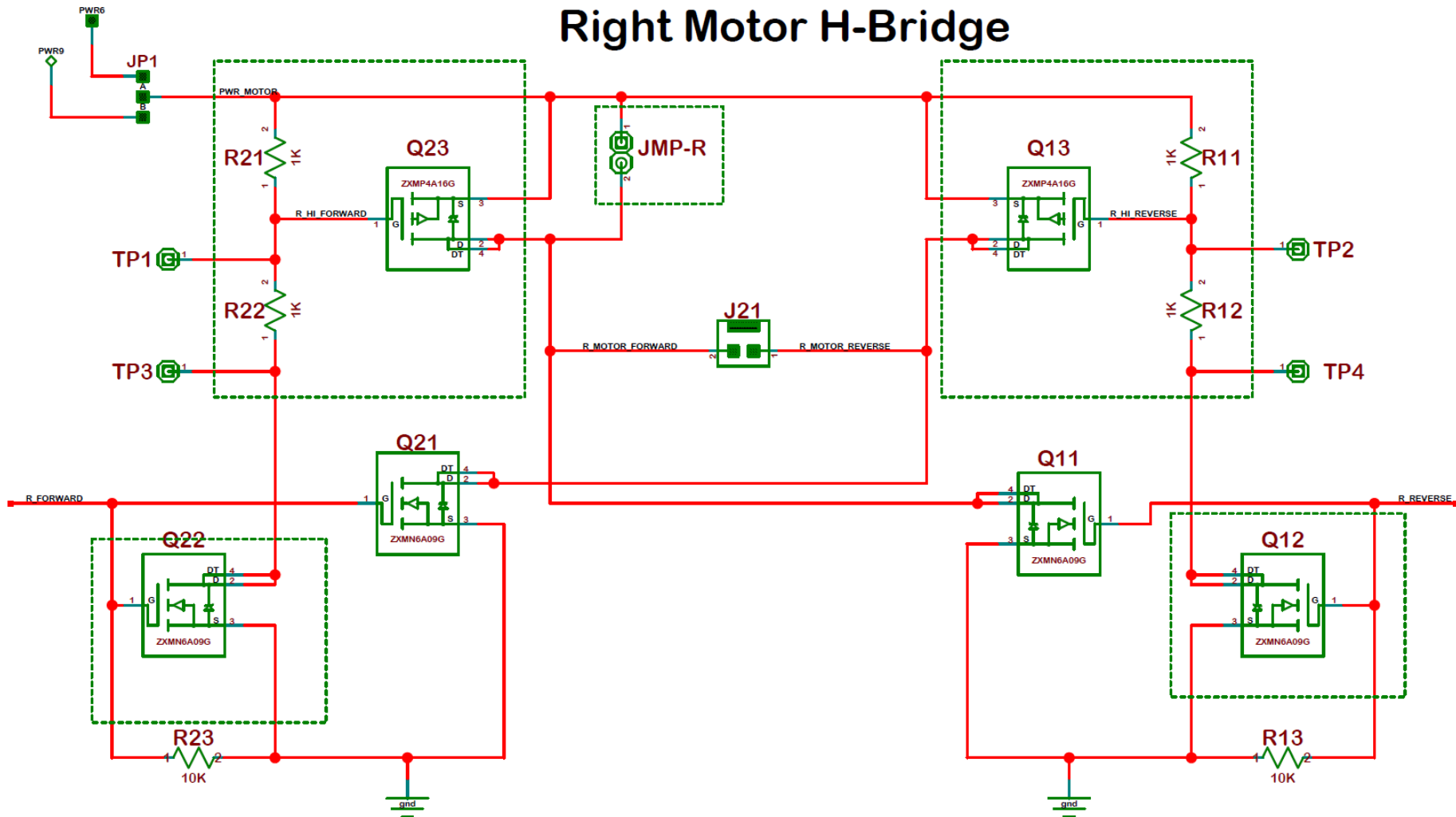


Schematics

Left Motor H-Bridge

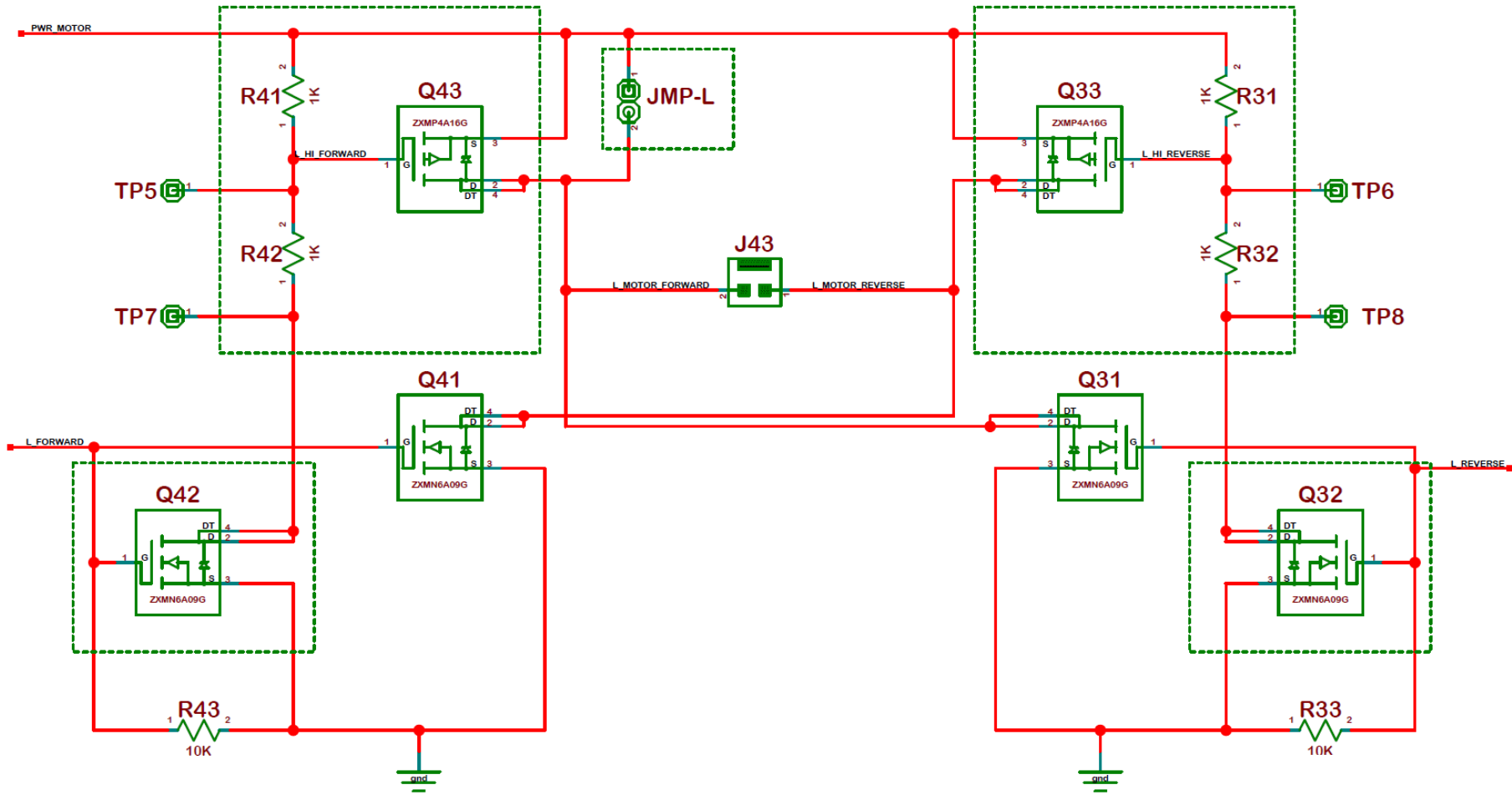


Schematics


Left Side Line Detect

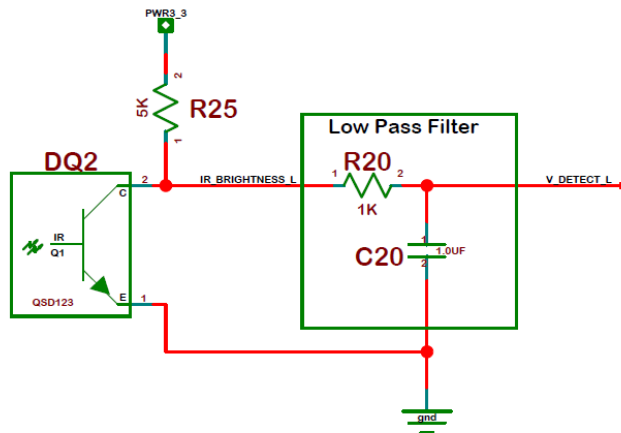

Center Emitter

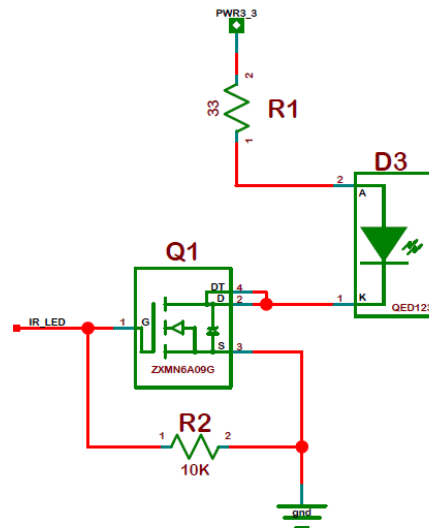


Right Side Line Detect

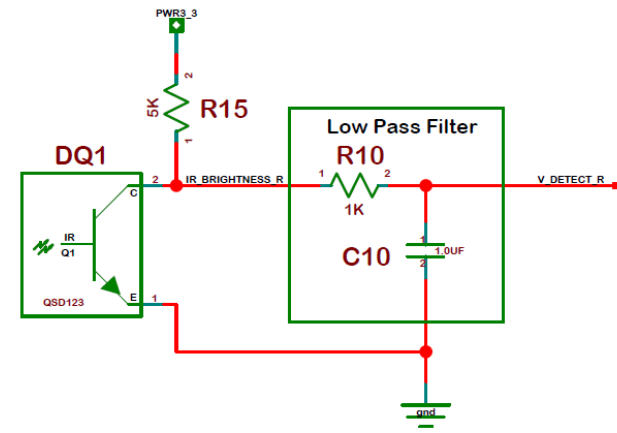


Schematics

Interconnect

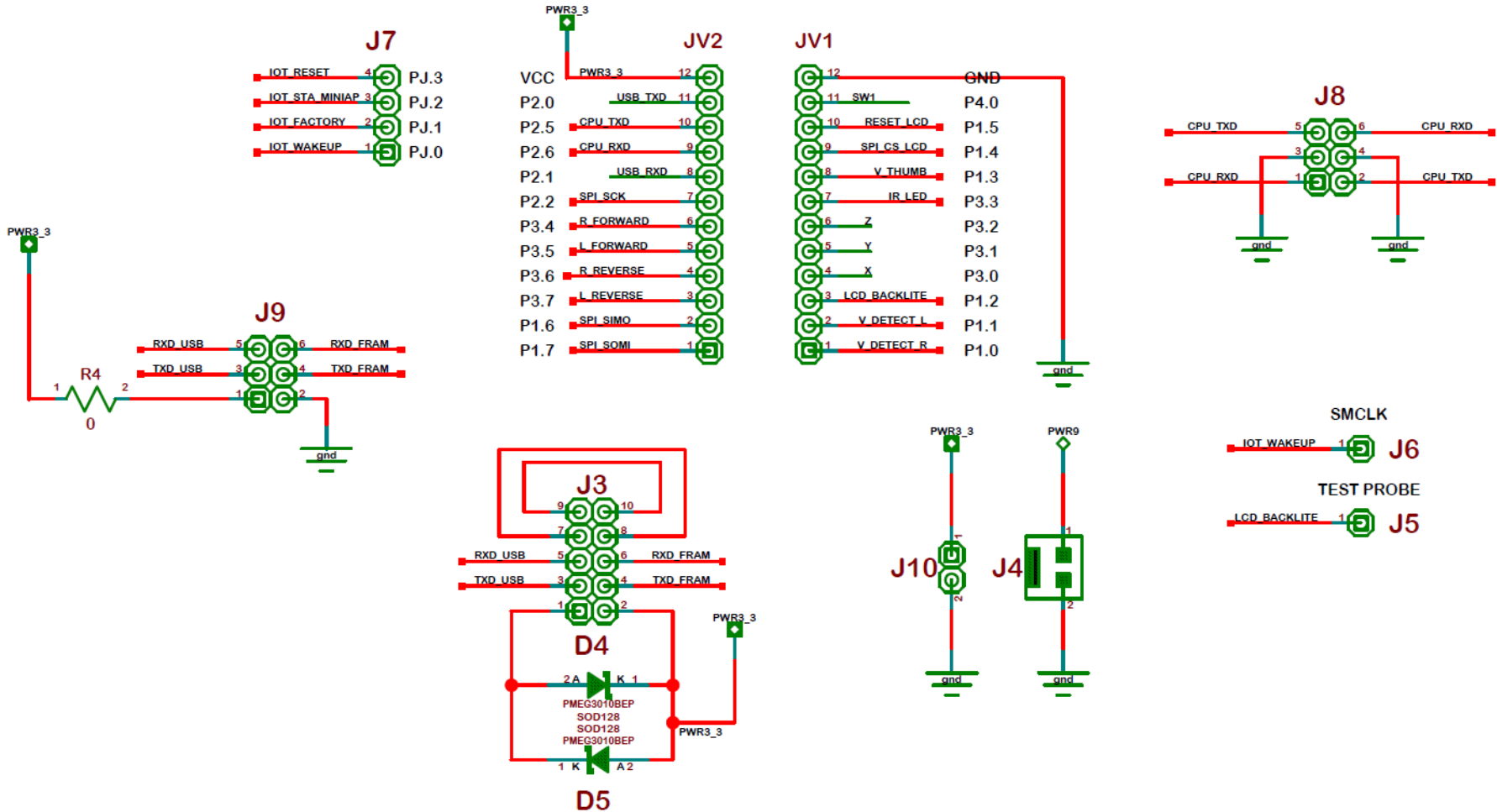


Schematics


LCD

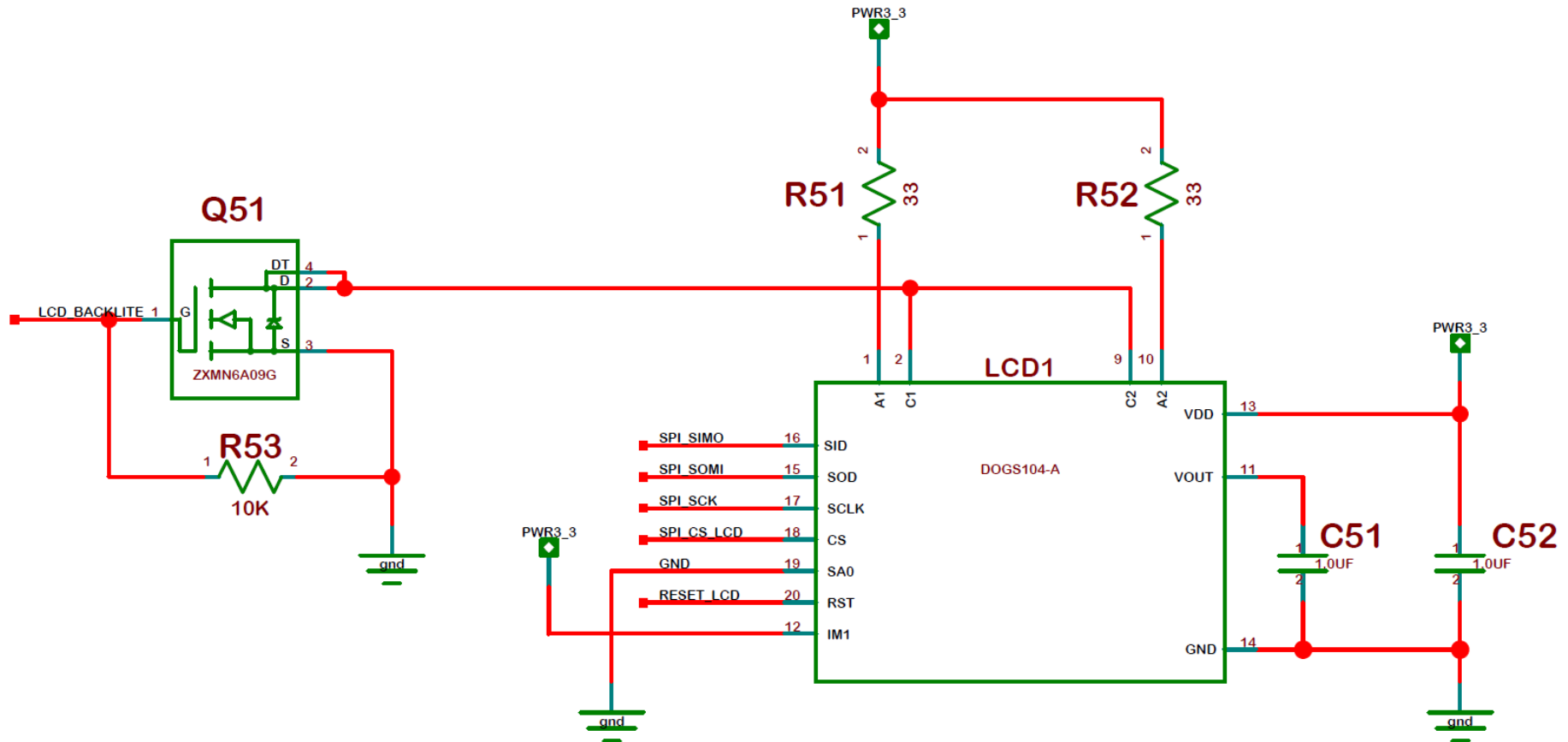

Schematics

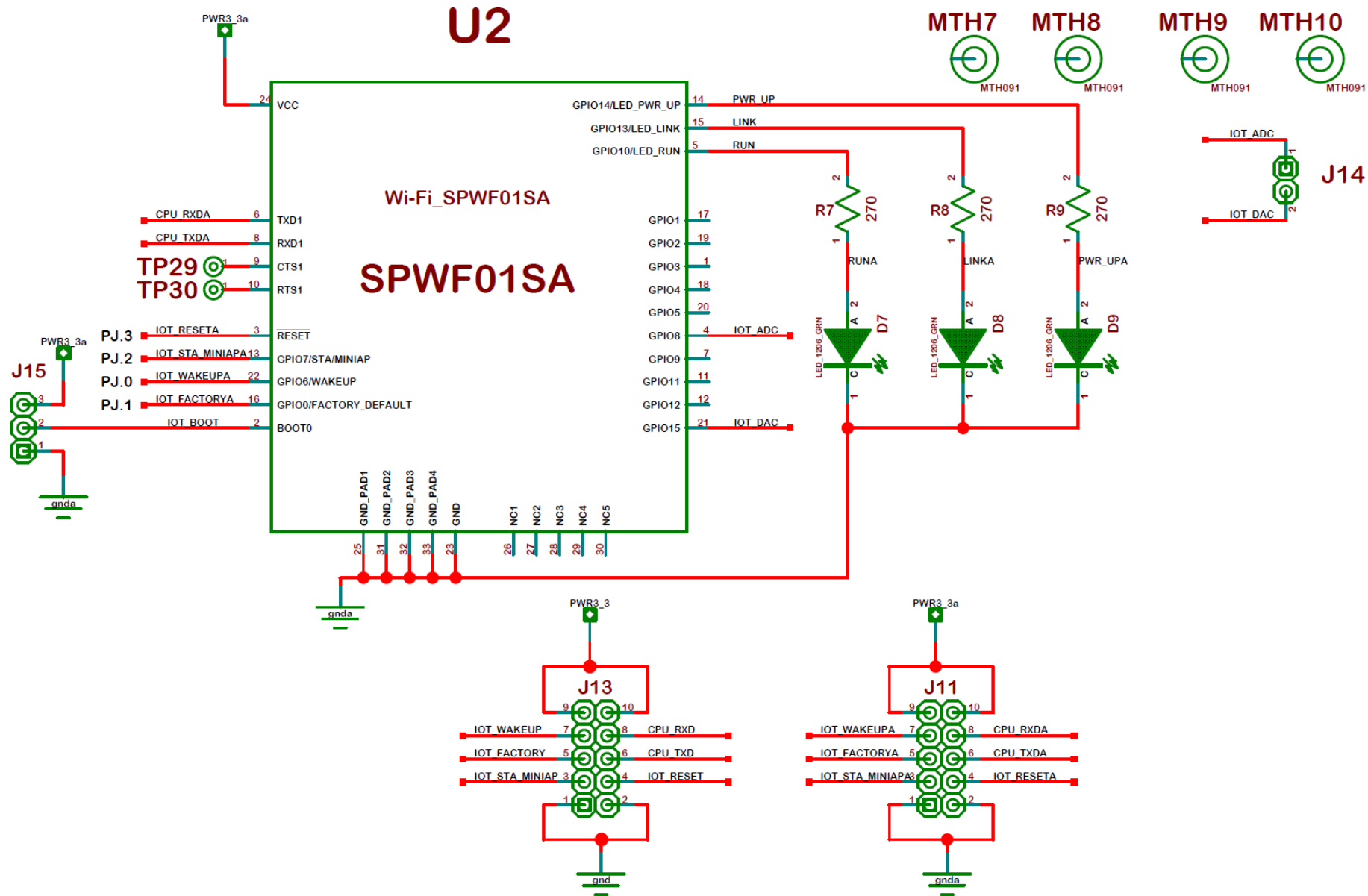

Schematics

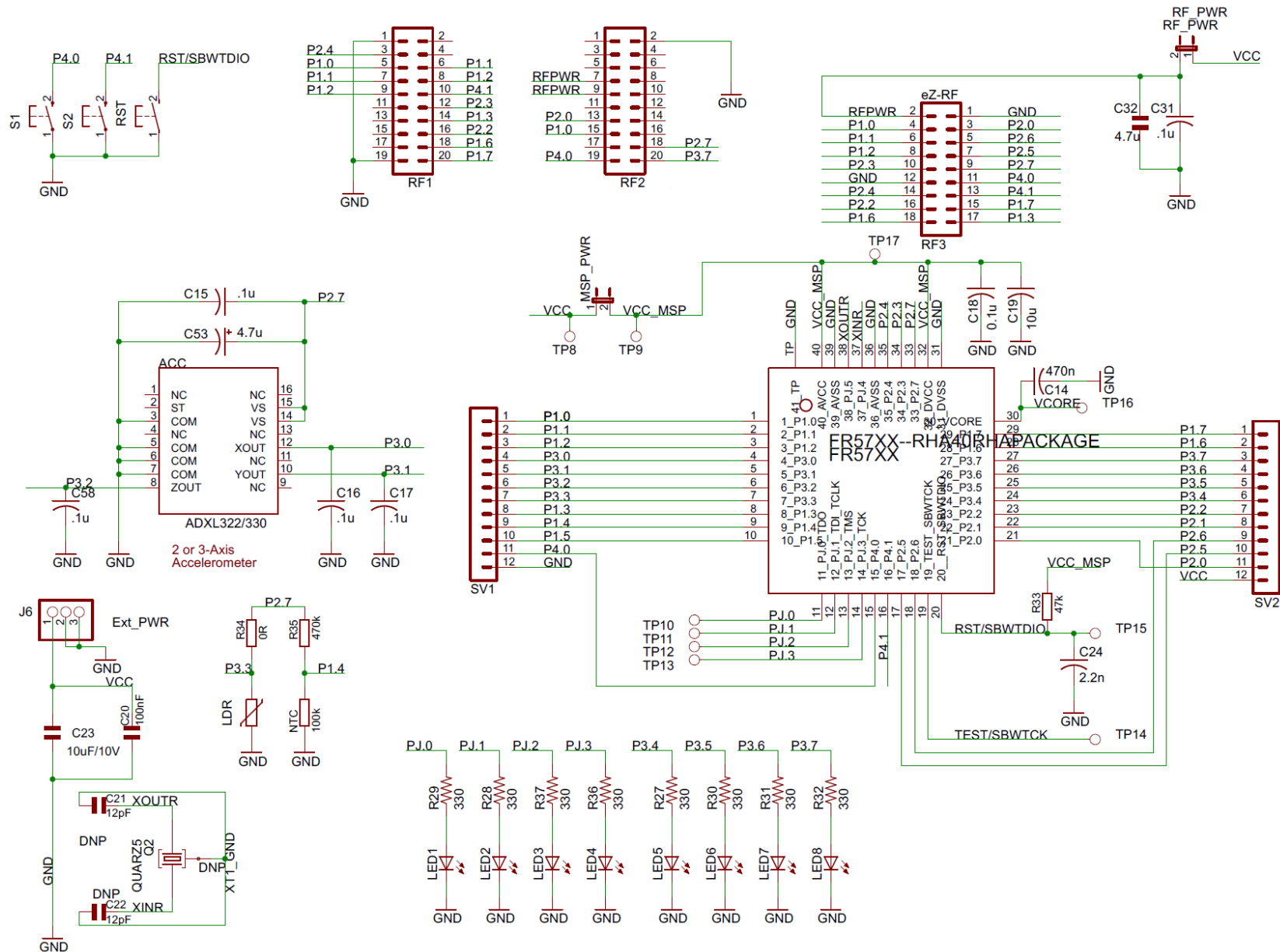

Schematics

- Project Template –
- Write-up Expectations –